

# CS/COE 0447

## Plexers and Simple Logic Minimization

wilkie (with content borrowed from:  
Jarrett Billingsley  
Dr. Bruce Childers)

# Exam:


- Pretty good.
- Half the class got an A.
  - Lenient grading to avoid some of your F's meant lots of A's. Boo.
  - Exam 2 is generally harder, in a fashion, imo, so I'm not worried. ☺
- Some notes:
  - $2^0 = 1$  (not 0!! I'm a tad concerned!!)
  - The smallest unsigned integer is 0, naturally. ( $2^0 - 1$ , if you must)
  - Some of you said largest is:  $2^{10} + 2^9 + 2^8 + 2^7 + 2^6 + 2^5 + 2^4 + 2^3 + 2^2 + 2^1 + 2^0$ 
    - True! But that's the same as  $2^{11} - 1$  so I hate it. ☺ (but you get credit anyway, but not on the final)

# Muxes, Demuxes, and Decoders

When you need particular data
 
# Hardware that makes decisions

- A **multiplexer (mux)** outputs one of its inputs based on a **select**.




This is the select input.

# What's that enable input?

- If you don't understand tristate buses or high impedance states, **turn off the *enable* input.**
- If you ever see **blue wires**, you are in weird, confusing territory.
- if you know this stuff, fine, but otherwise...

## Selection: Multiplexer

Facing	East
Select Location	Bottom Left
Select Bits	1
Data Bits	4
Disabled Output	Floating
Include Enable?	No

 


- I want a circuit that does this:

```
if(select == 1)
    output = A - B
else
    output = A + B
```

- Let's see what that looks like
- A mux is like a **hardware if-else statement**
- But unlike in software...
  - The "condition" comes at the "end" (the output)
  - Instead of doing one *or* the other, we **do both, choose the one that we care about, and ignore the rest!**

 
# Demultiplexers

- A **demux** does the opposite: it sends its input to one of its outputs
- **The rest of the outputs are 0s**


 
# Looking in a mirror

- it can be confusing if all you see is this:




Logisim distinguishes these, and  
I'll try to too, with arrows


 
# Decoders

- A **decoder** is like a 1-bit demux whose input is always 1



exactly one output is 1,  
and the rest are 0s

# Uses for decoders and demuxes

- Unless you're using tristate (blue) wires, they're not too useful...
- They let us create data buses and such.
  - Lets many stateful components share data wires, essentially.
  - It's a nice optimization, but we don't *have to* do this.
- Most of the time, you don't have to "direct" a signal to a location.
  - Instead, you **hook up the inputs to everything that needs them**.
- Since these are more about encapsulating state, we'll use them more when we get to **sequential logic**.

# Combinational vs Sequential Logic




- **Combinational logic:** the outputs of a circuit depend entirely on their **current** inputs
  - AND, OR, NOT, XOR gates
  - adders
  - muxes, demuxes, and decoders
  - Basically: It converts an input to an output in one go.
- **Sequential logic** is coming up soon
  - the outputs can depend on the **current and previous** inputs
  - it *remembers*
  - Basically: It actually computes: the process changes the state of the machine, which in turn changes *how* it converts input to output.
  - Built from sections of combinational logic.
- Logic minimization techniques only work on **combinational** logic!
  - ...or combinational *pieces* of a larger sequential circuit

# How ICs are made

(another For Fun™ section)

  
 
# How ICs (integrated circuits) are made

- silicon is purified and grown into a **monolithic crystal** (*extremely expensive*)
- this is sliced thinly to make **wafers**
  - gooey caramel is put between them to make **stroopwafel**
- a series of complicated photochemical processes do things like:
  - change its electrical properties
  - make wires to connect things
  - make inert insulating layers


  
# How ICs (integrated circuits) are made

- many ICs are printed on one wafer
- the wafers are **diced** (chopped up)
- the ICs are **tested**
- the ICs are **mounted** in a package →
- they're tested *again*
- *then* they're ready to sell



# Manufacturing yield

- ICs are **tiny and complex**
- silicon crystals can have **defects**
- a tiny speck of dust during production can **ruin an entire chip**
- the **yield** is the **percentage of usable chips**
  - **bigger** chips have **smaller** yields: more opportunities for mistakes!
- the **size of the silicon** is **the biggest factor** in the price of an IC
  - huge ICs (several *cm* on each side!), such as very high-resolution camera sensors, can cost **tens of thousands of dollars!**
- manufacturers can also **bin** resulting chips
  - bug-free ones can be sold as Core i7s for *lotsa money*
  - slightly malformed ones can be sold as Core i5s and i3s
  - the ones they sweep off the floor are the Celerons

# Logic Minimization

Making Smaller Circuits





# Silicon is expensive, rocks are slow

- **logic minimization** means using the **smallest number** of gates/transistors possible to implement a boolean function
  - a **boolean function** is anything we've talked about
  - it has boolean inputs, and boolean outputs
- fewer transistors means:
  - smaller area:
    - **cheaper chips!**
    - **more stuff** on one chip!
    - **smaller chance** of manufacturing **defects!**
  - less gate delay:
    - **faster circuits!**
  
# A first try

- Let's make a truth table for a **two-input 1-bit multiplexer**.



S	A	B	Q
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

# I Couldn't Even Care One Bit

- We don't even *care* about the *unselected* input
- We can put **X** in the inputs we don't care about
- We call these **don't cares**
  - yep, really
- What these mean is:
  - when we make this into a boolean function, we can **ignore** those inputs
    - we won't even need to write em

S	A	B	Q
0	0	X	0
0	0	X	0
0	1	X	1
0	1	X	1
1	X	0	0
1	X	1	1
1	X	0	0
1	X	1	1

# Making a Boolean Expression

- Let's make a boolean expression from the truth table:

- find all rows with an **output of 1**
- for each one, write an AND of all the inputs, with NOTs on the 0s
- eliminate duplicate terms
- OR the remaining terms together


$$Q = \bar{S}A + SB$$

- This is what we call a **sum-of-products**
  - An OR of multiple ANDed terms

	S	A	B	Q
	0	0	X	0
	0	0	X	0
$\bar{S}A$	0	1	X	1
<del><math>\bar{S}A</math></del>	0	1	X	1
	1	X	0	0
$SB$	1	X	1	1
	1	X	0	0
<del><math>SB</math></del>	1	X	1	1
 
## Turning that expression into gates

- making  $Q = \bar{S}A + SB$  into gates is pretty straightforward:



## Limitations of the last method

- If we use that method on the **C<sub>0</sub>** of a full adder:

$$\mathbf{C}_{\text{out}} = \overline{\mathbf{A}}\mathbf{B}\mathbf{C}_{\text{in}} + \mathbf{A}\overline{\mathbf{B}}\mathbf{C}_{\text{in}} + \mathbf{A}\mathbf{B}\overline{\mathbf{C}_{\text{in}}} + \mathbf{A}\mathbf{B}\mathbf{C}_{\text{in}}$$

A	B	C <sub>in</sub>	C <sub>out</sub>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$\overline{A}BC_{in}$$
$$A\bar{B}C_{in}$$
$$\overline{ABC_{in}}$$

# ABC<sub>in</sub>

- [illegible]